

Micro-Needle Camera with a 2-Wire Interface


Abdullah Saboor, B J Roxane

Ouango, Qijia Li, Yanwen Zhu

Cornell University


What is a needle camera?

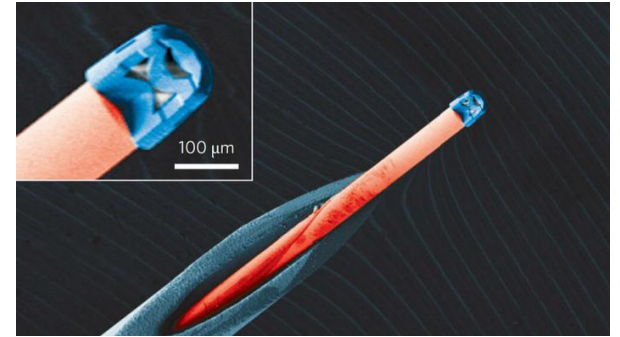- Initially, endoscope procedures were largely limited to the throat and other large passageways. Now, you can use tiny cameras mounted on needles to examine other parts of your body.
- Needle cameras have applications ranging from diagnosis all the way to surgical procedures.
- Needle cameras can also be used for 3D modelling of internal structures such as blood vessels.



Why a 2-wire interface?

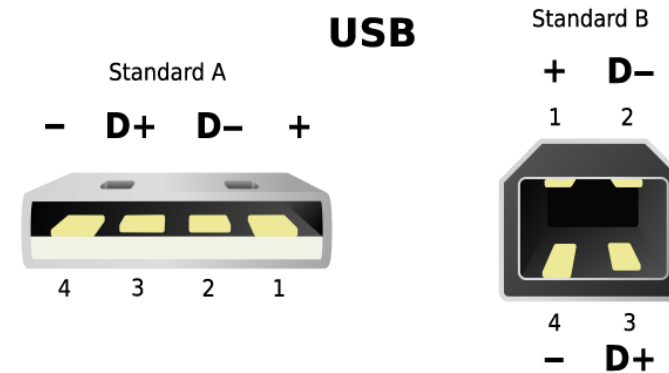- Generic communication interfaces use 4-wire interfaces with two wires carrying the signal and two wires carrying power.
- Cannot be used for a micro-needle camera as DC currents cause chemical reactions resulting in corrosion of wires.
- Also want to minimize the wires in contact with the body.




- Need some way to integrate power and data onto the same wires.
- One way: Frequency-Division Multiplexing
(HF Power combined with LF Data Signals)

Design Goals


- 8-px resolution.
- Data transmission over the two wires.
- Power Optimization and reduce complexity.
- Make it work altogether.

Micro-needle Camera Design Overview

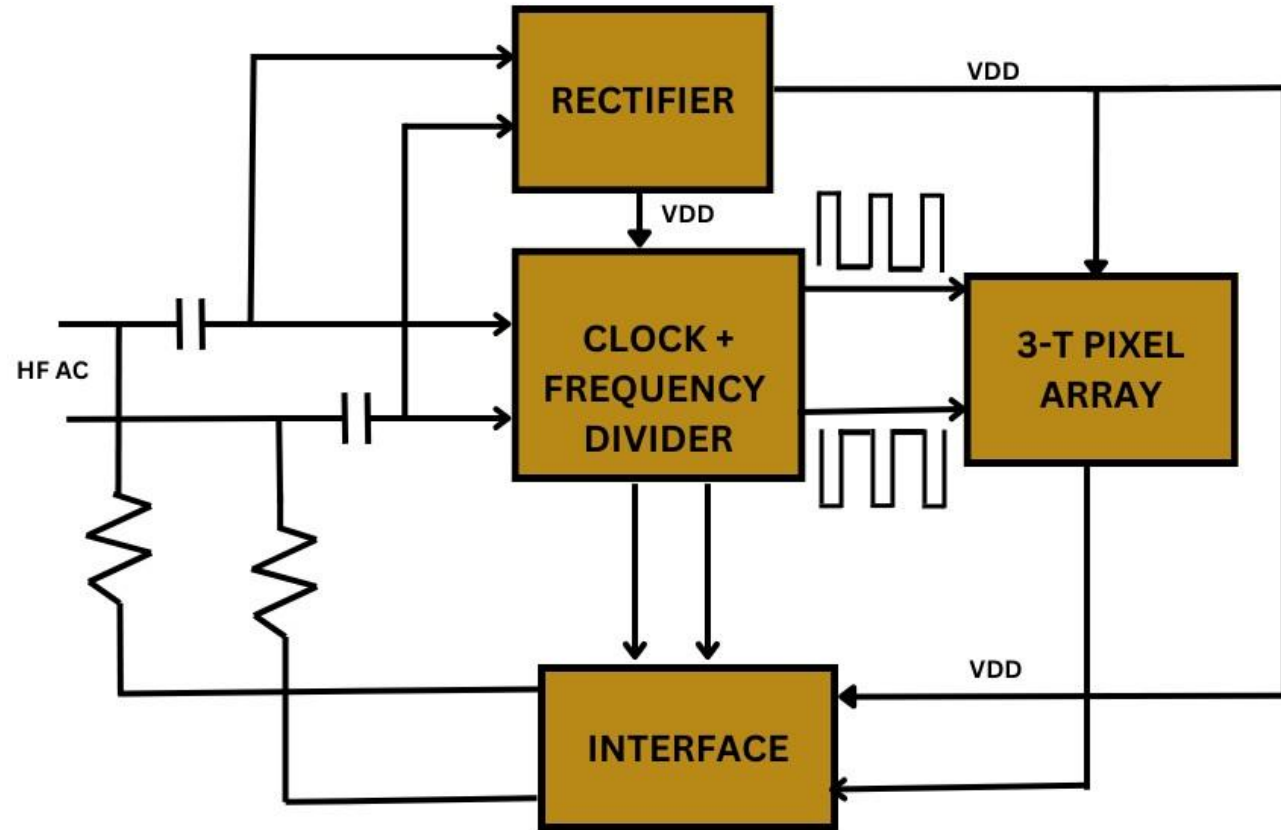


CMOS Rectifier

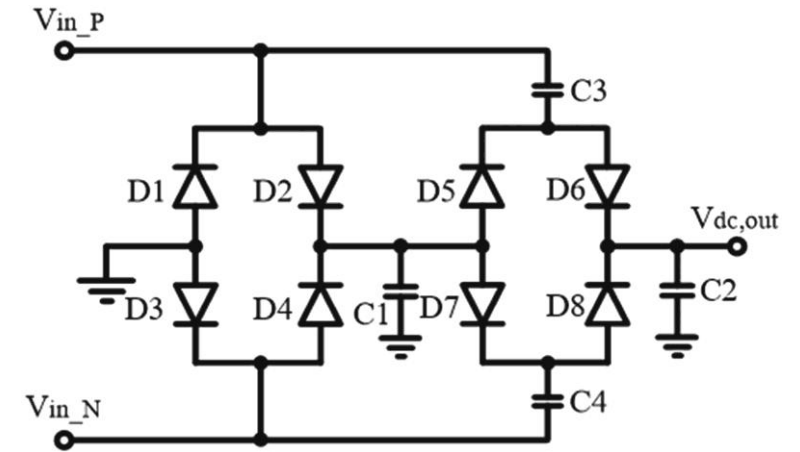- CMOS rectifier has no voltage drop unlike the diode bridge rectifier.
- Can be cascaded together to provide a larger rectified voltage.
- Can give multiple DC voltage tap-out points.
- The current capability can be increased by increasing either frequency or the capacitances C3 and C4.





(A)

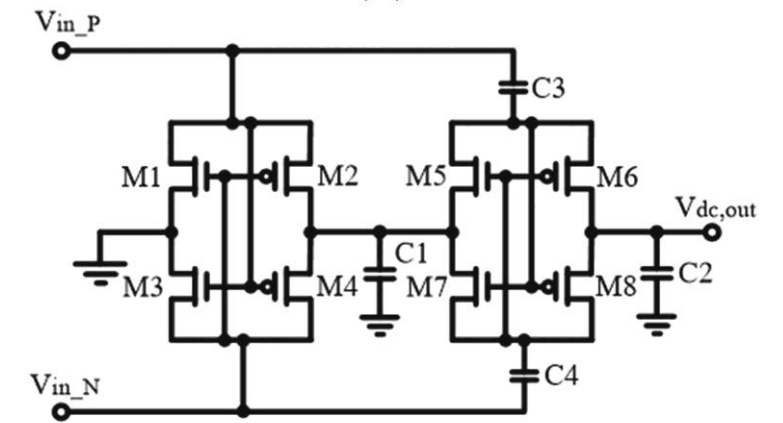

(B)

CMOS Rectifier Implemented – 3 Stage

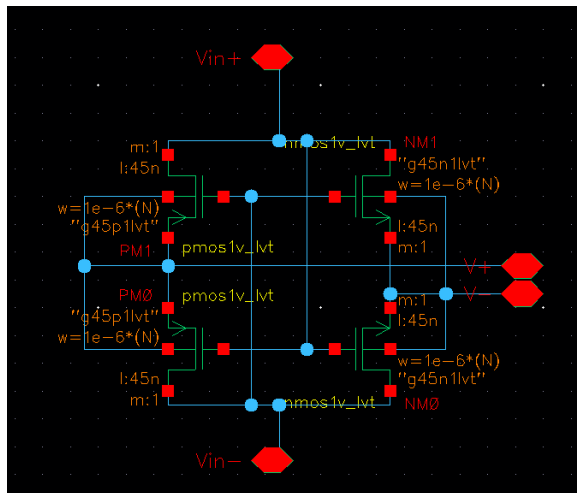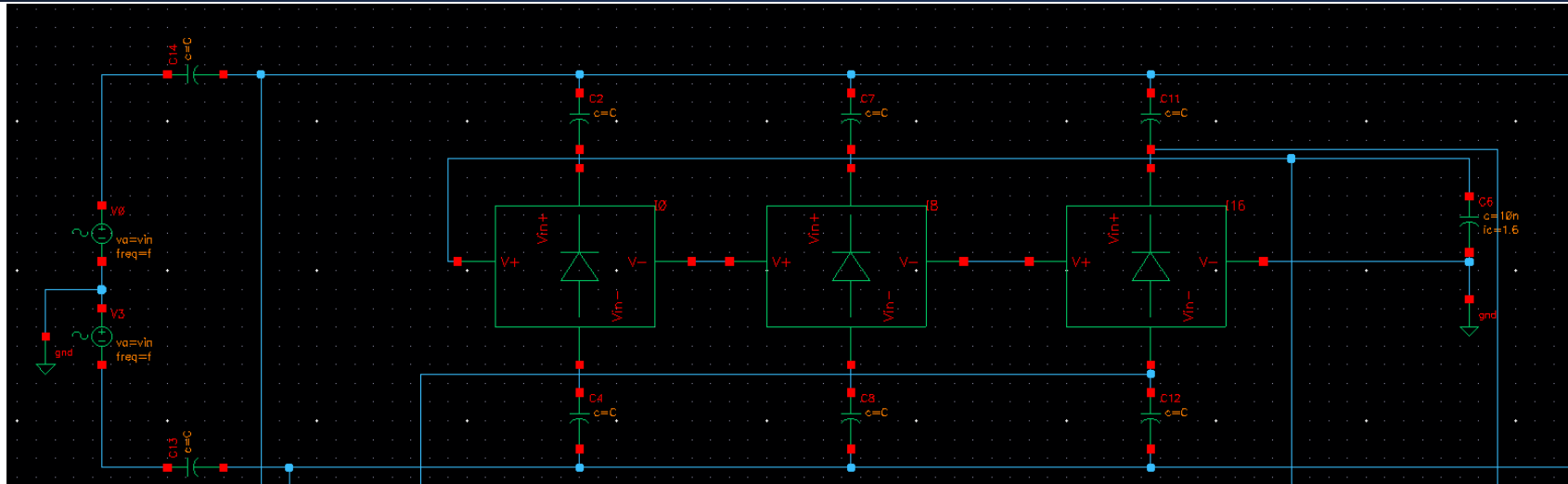


VDD Steady State Value = 2.23V



Transient Response

Name

v_dd

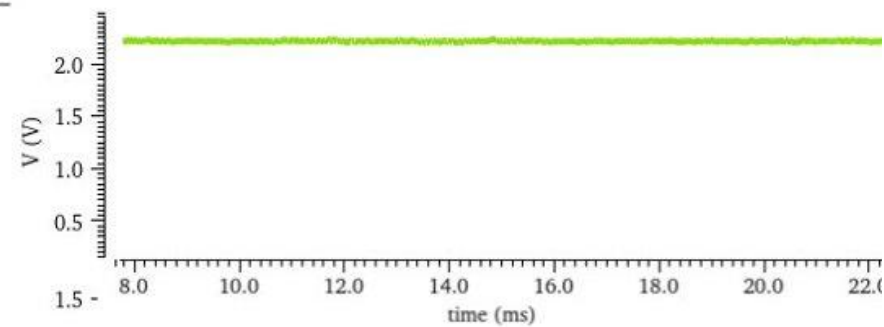

Clock Circuit Design

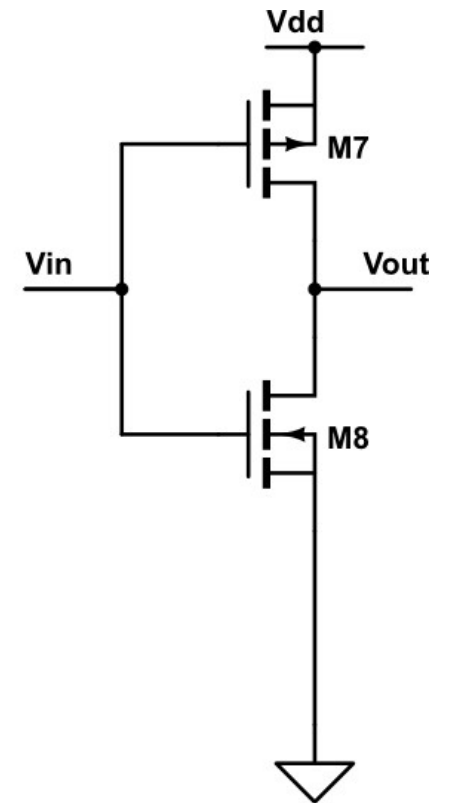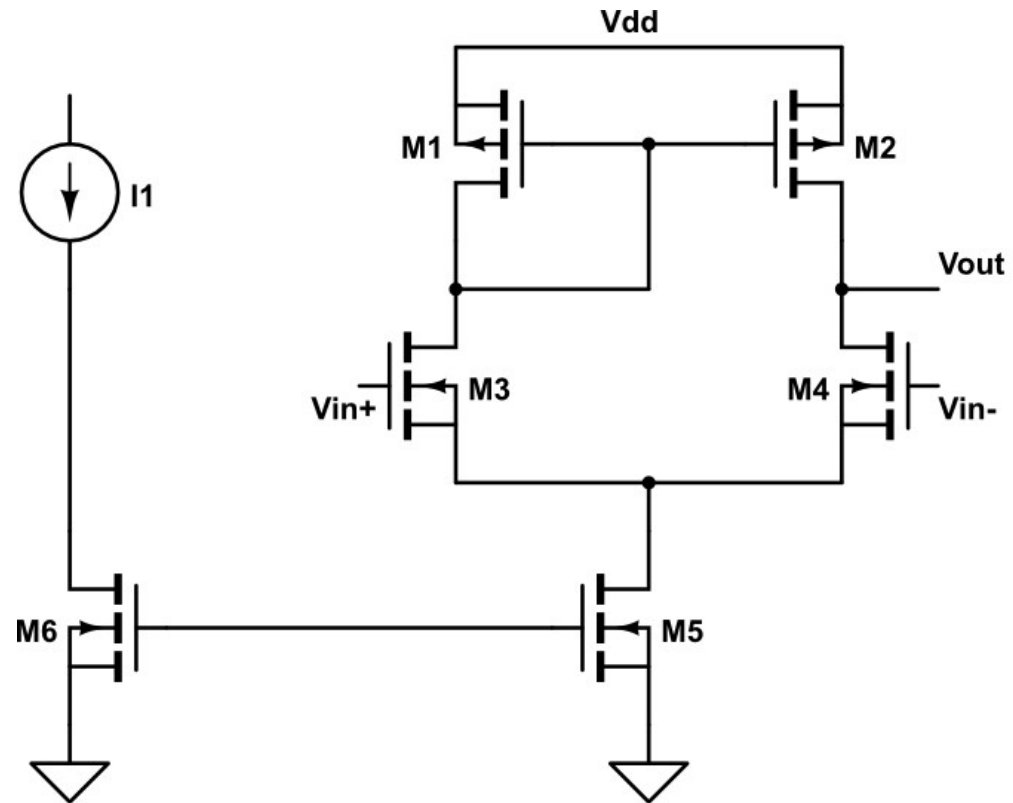

Generated Clock Pulses

Transient Response


Name

v /net6; tran (V)

v /net7; tran (V)

v /net9; tran (V)

v /net8; tran (V)

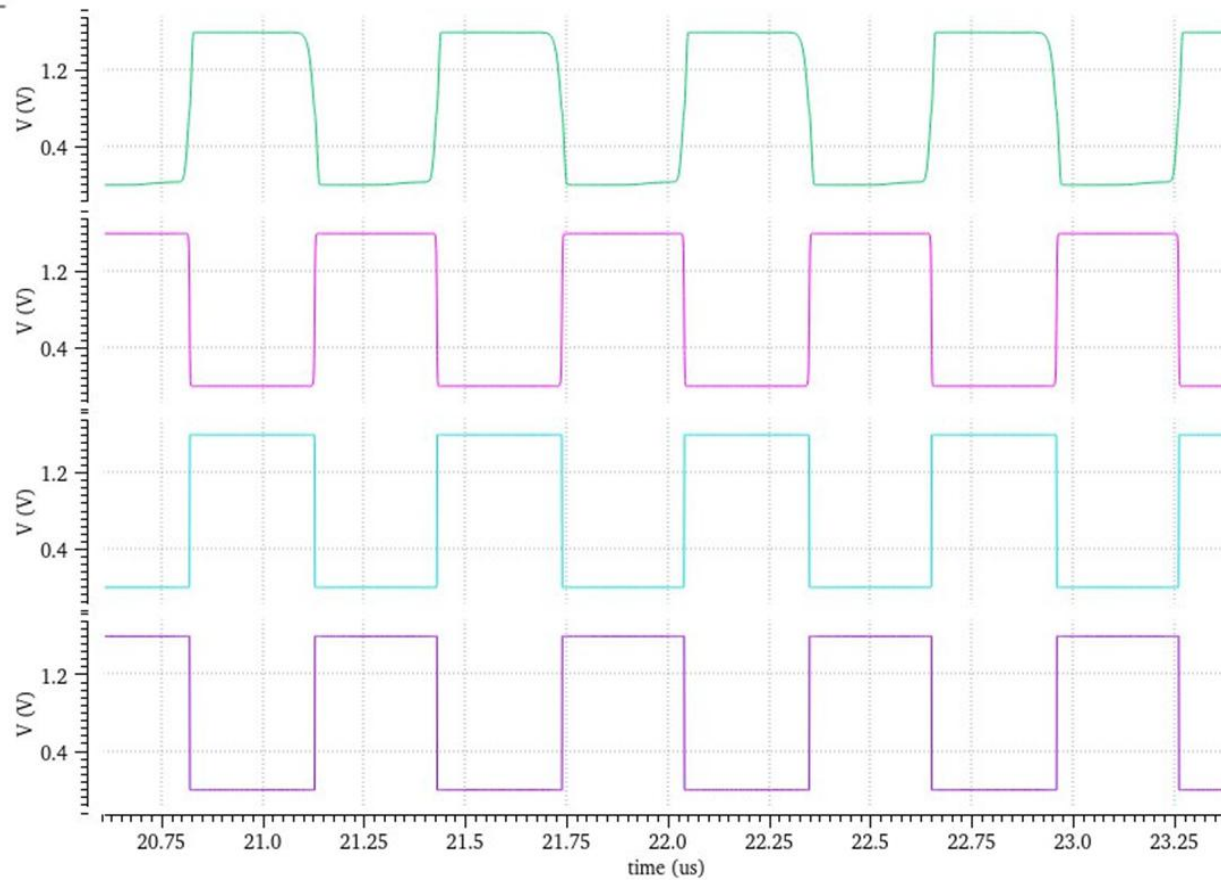

1


← Diff Pair Output

← First Inverter

← CLK


← CLK

Frequency Divider

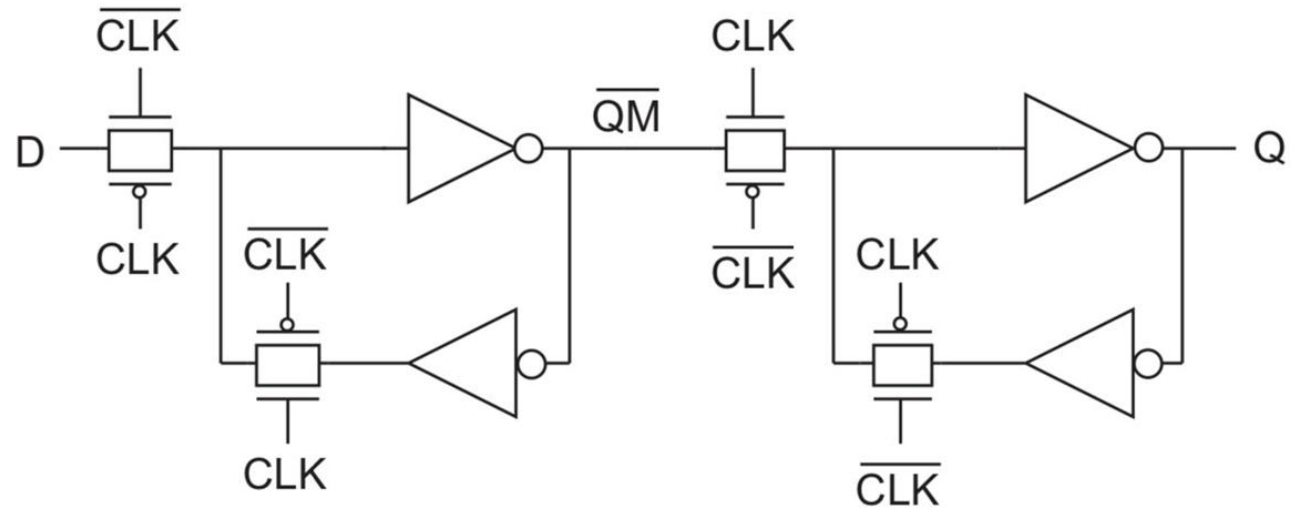


- D flip-flop: divide the frequency by 2
- 14 flip flops: divide the frequency from original 1.6384MHz to 100Hz

Clock Divider

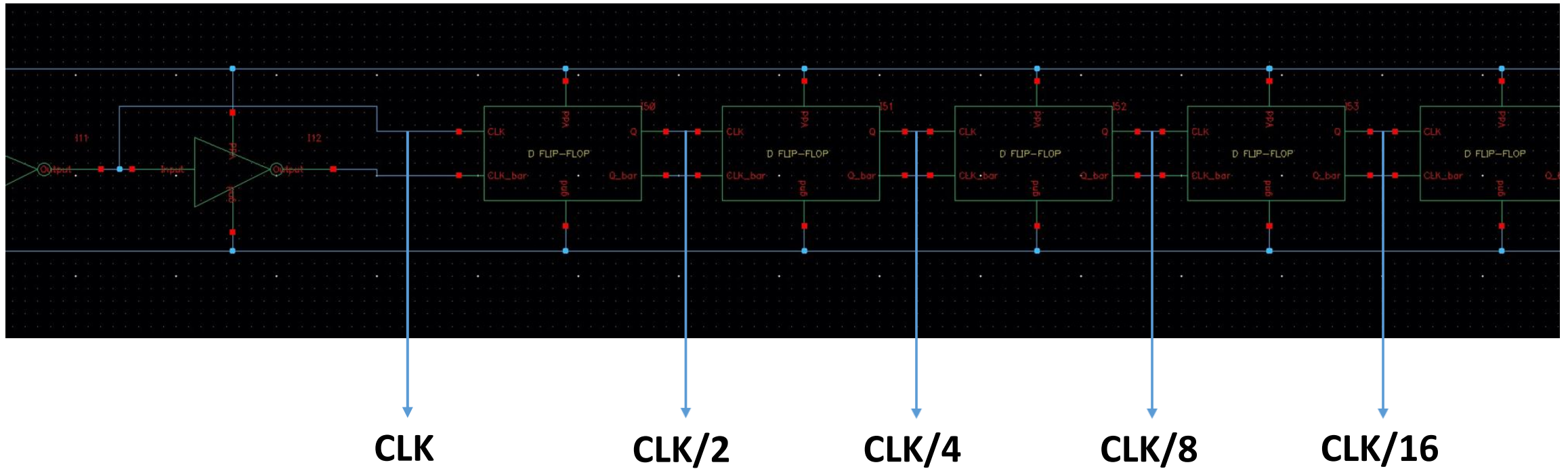


Generated Clock Pulses

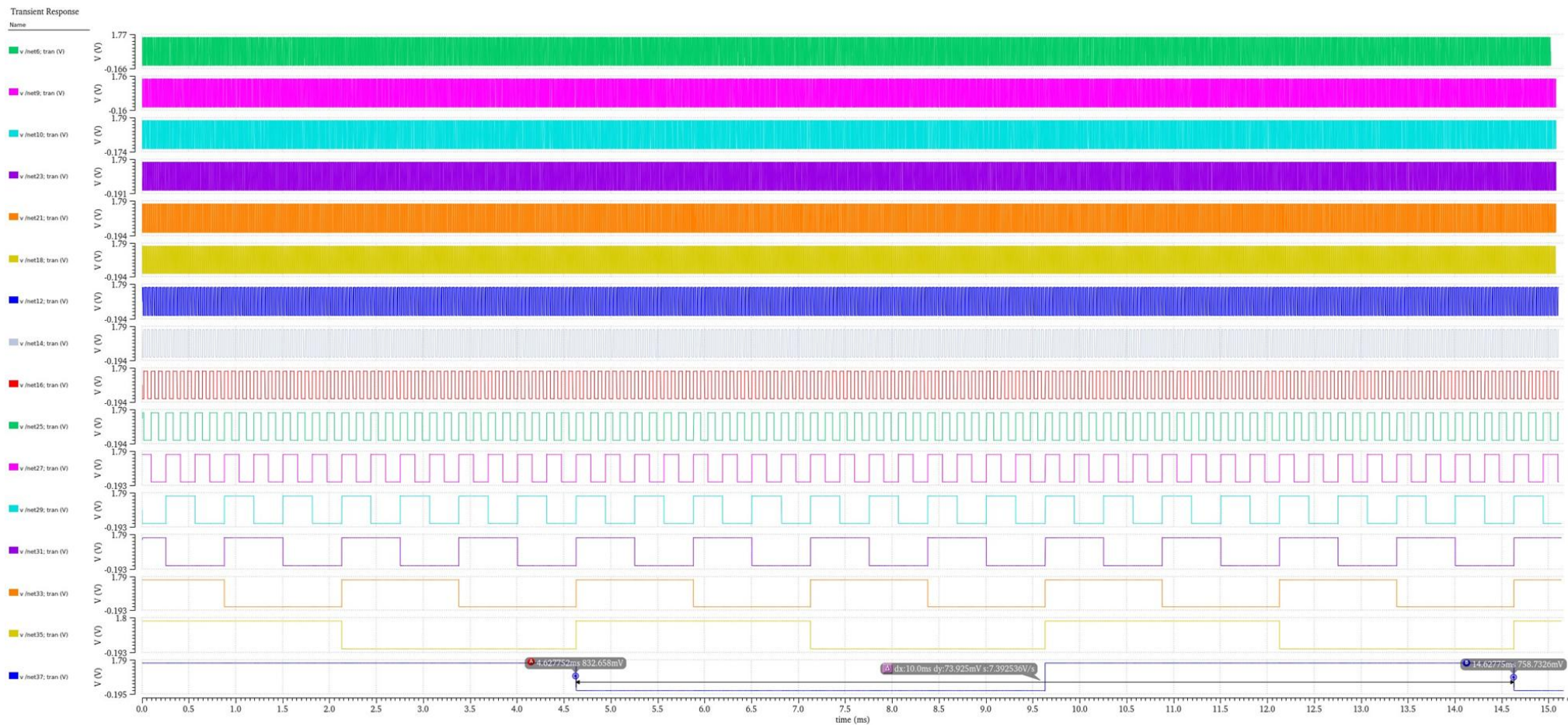

Performance Evaluation


Transient Response
Name

v_in[1]: tran (V)

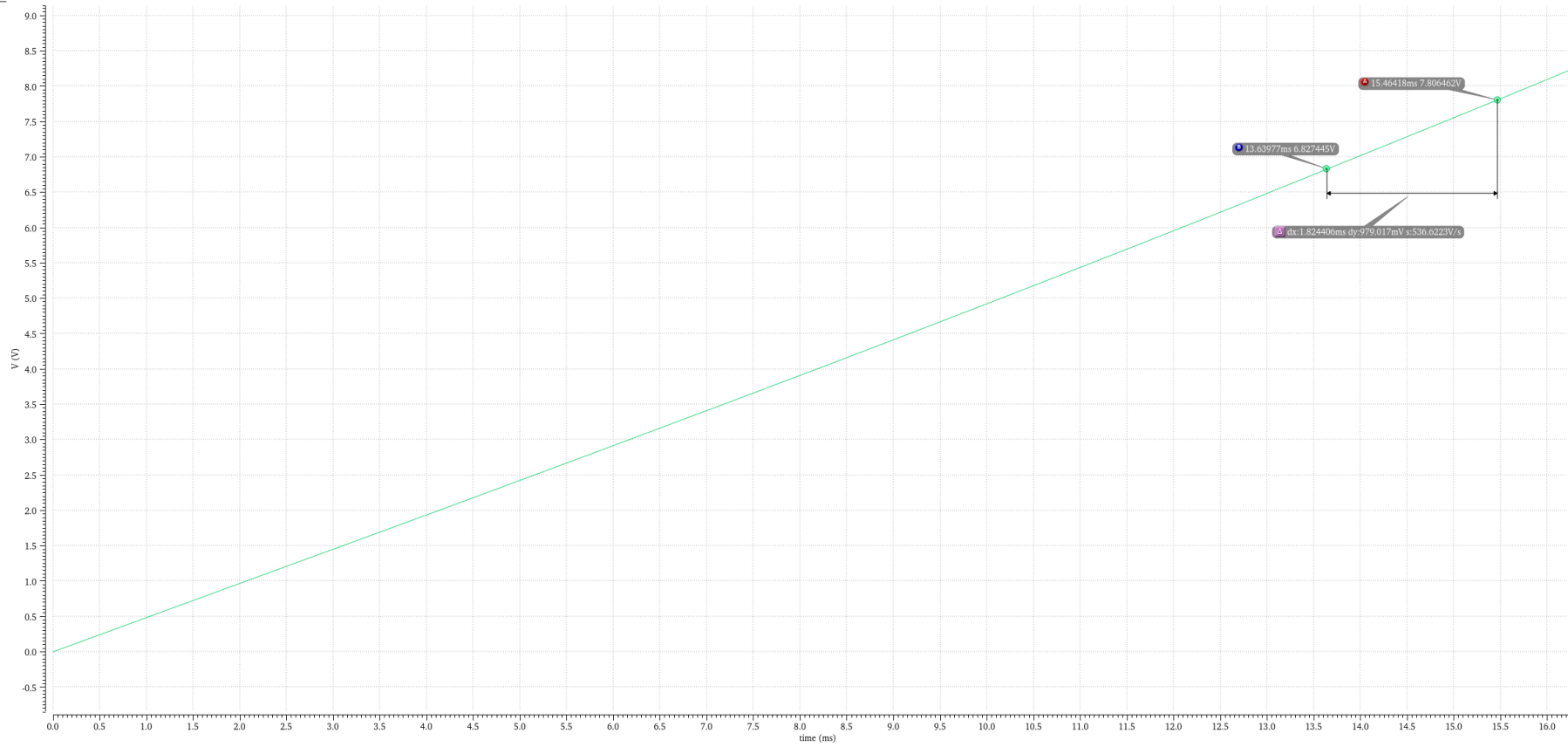


- Cap = 1n F
- Average Current = 0.53 μ A
- Power = 0.85 μ W

3-Transistor Pixel

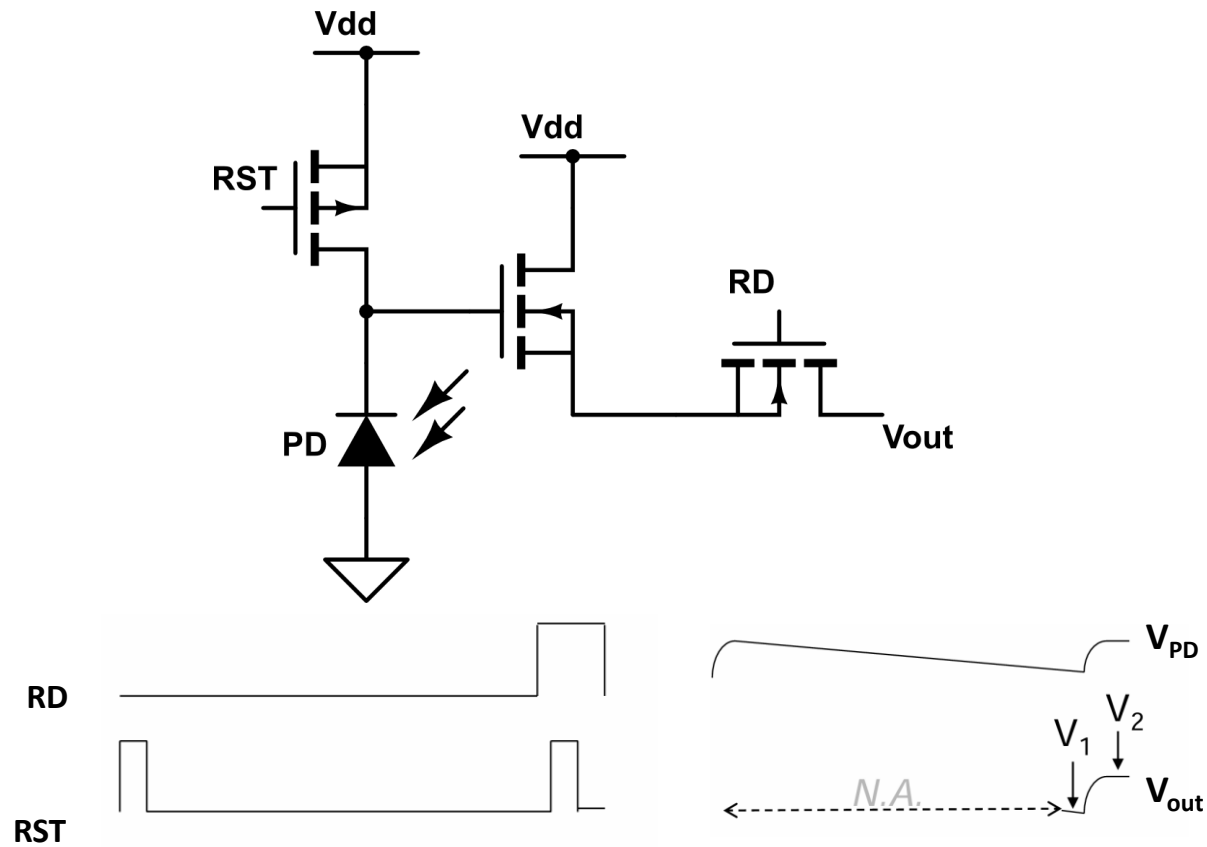

- Reset Transistor (RST)
 - Pre-charge the photodiode to starting voltage V_{RST}
- Source follower(SF) transistor
 - Amplifies the final output current
- RD Transistor
 - Outputs the value of the circuit when selected
- Photodiode(PD)
 - $V_{PD_RST} = V_{DD} - V_{TH(RST)}$

8-Pixel Design Overview

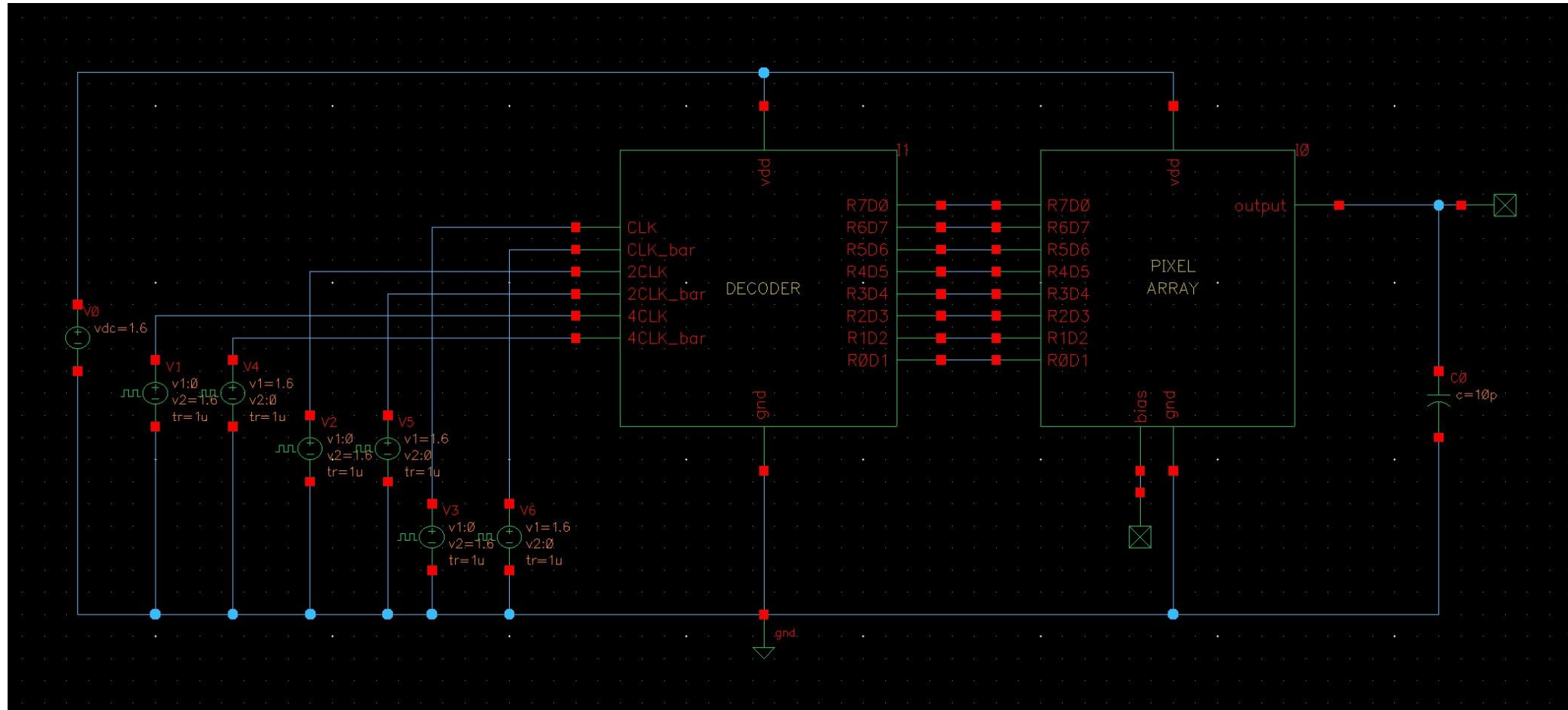

Single 3-Transistor Pixel Simulation


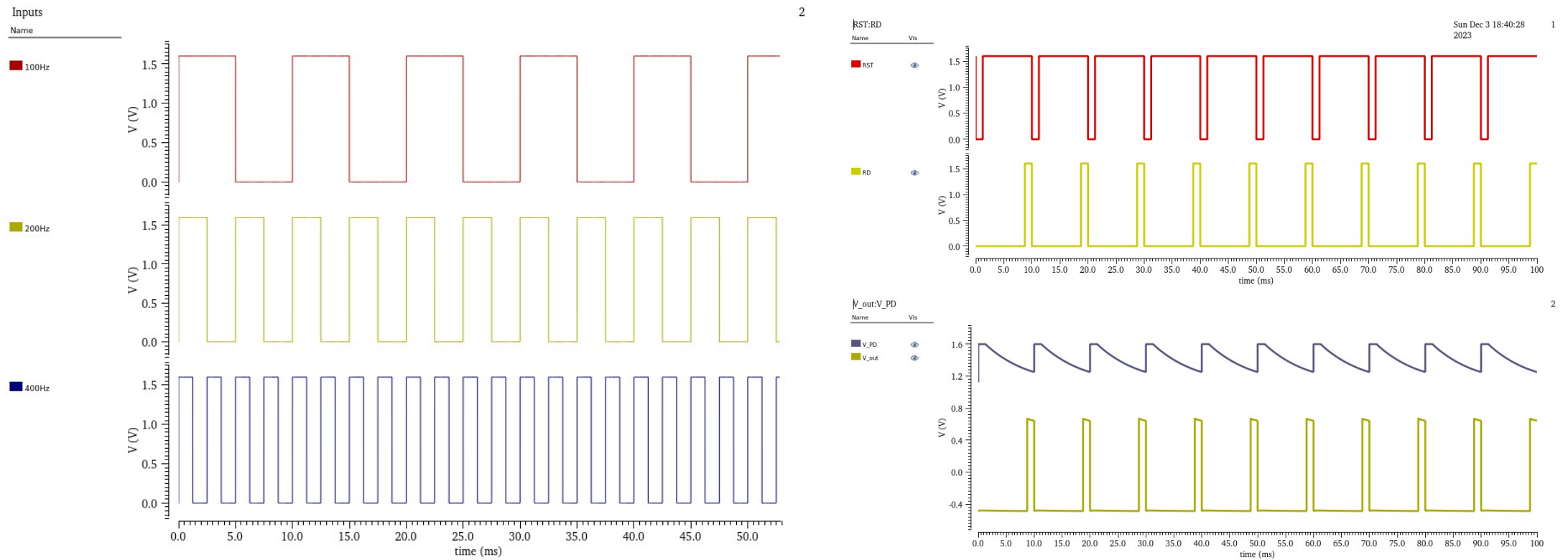
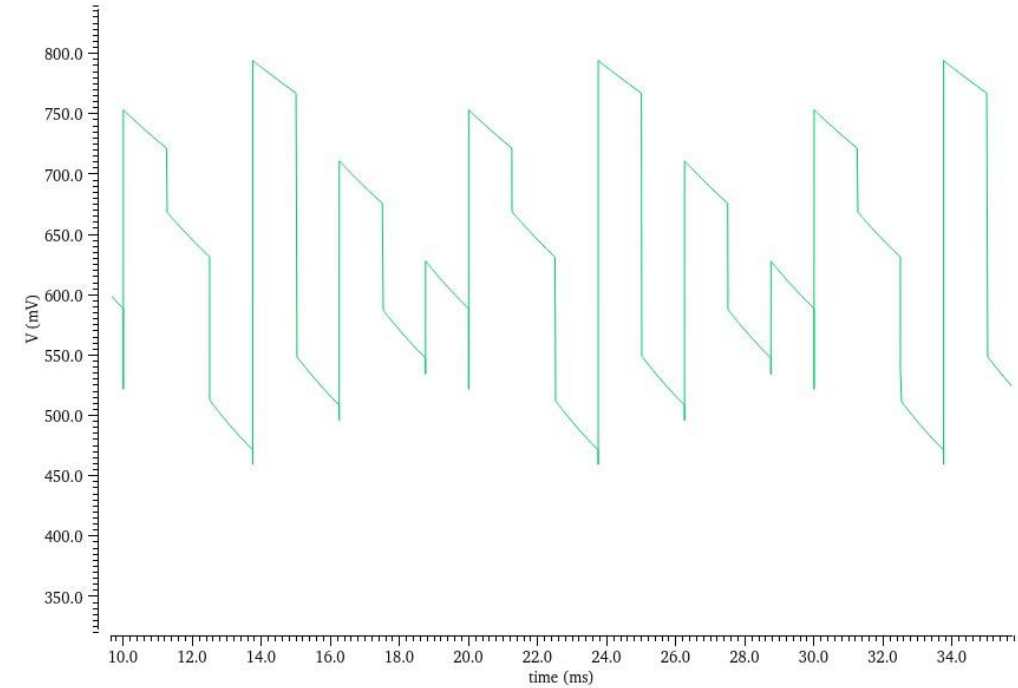


Figure 3: Active Pixel Inputs and Outputs



Decoder - 8 Pixel Simulation

1

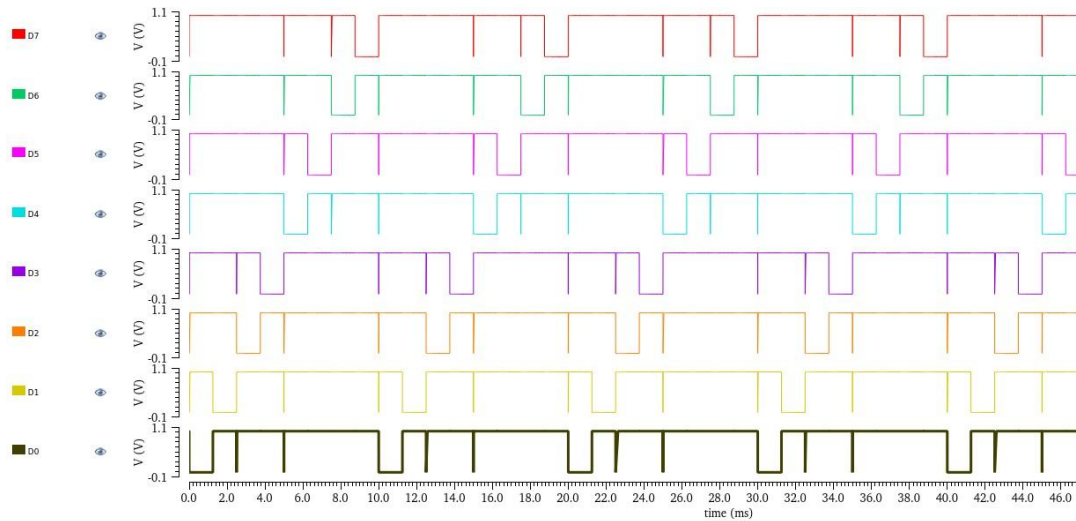



- Read N
- Reset N-1

Interface

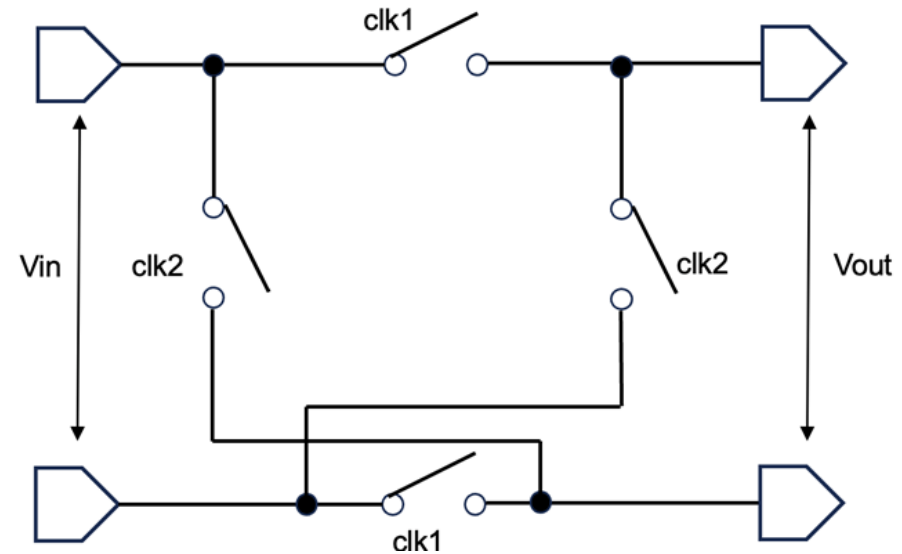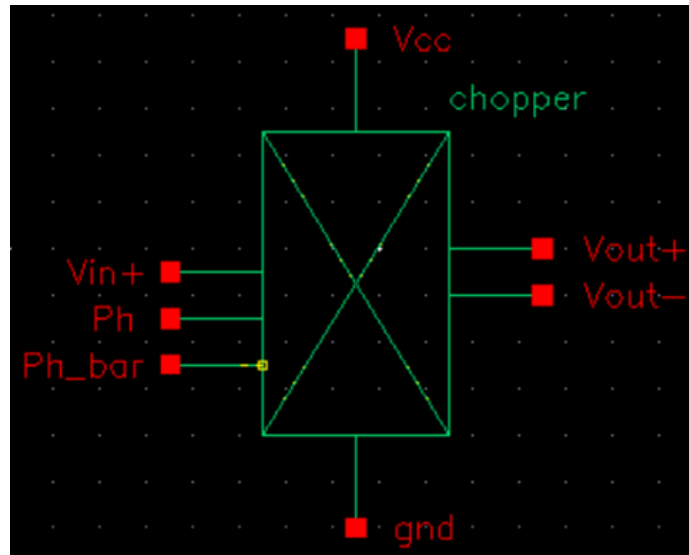


- provides inverting and non-inverting signal separately
- Two inverted clocks control the MOS transistor switches to exchange differential input signals

Interface Implementation

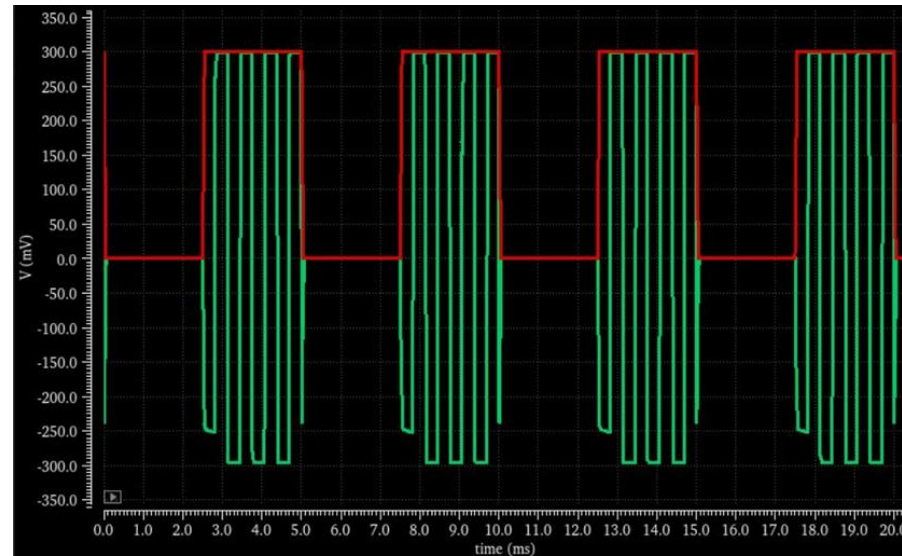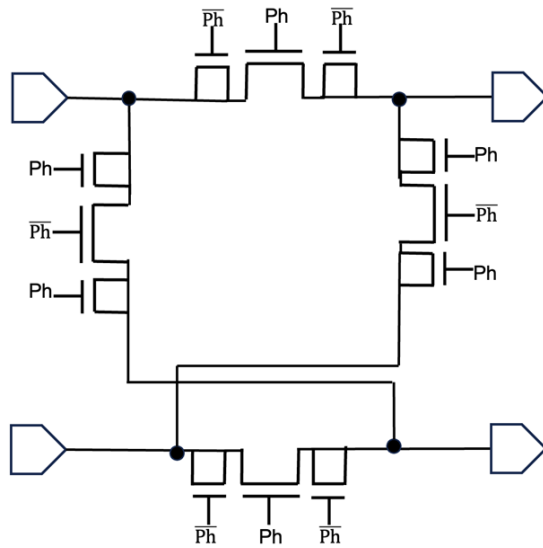

- Dummy Switch: Its clock is opposite to that of the main switch
- When the main switch is turned off, the leaked charge is absorbed by the open switches on both sides

Complete Schematic

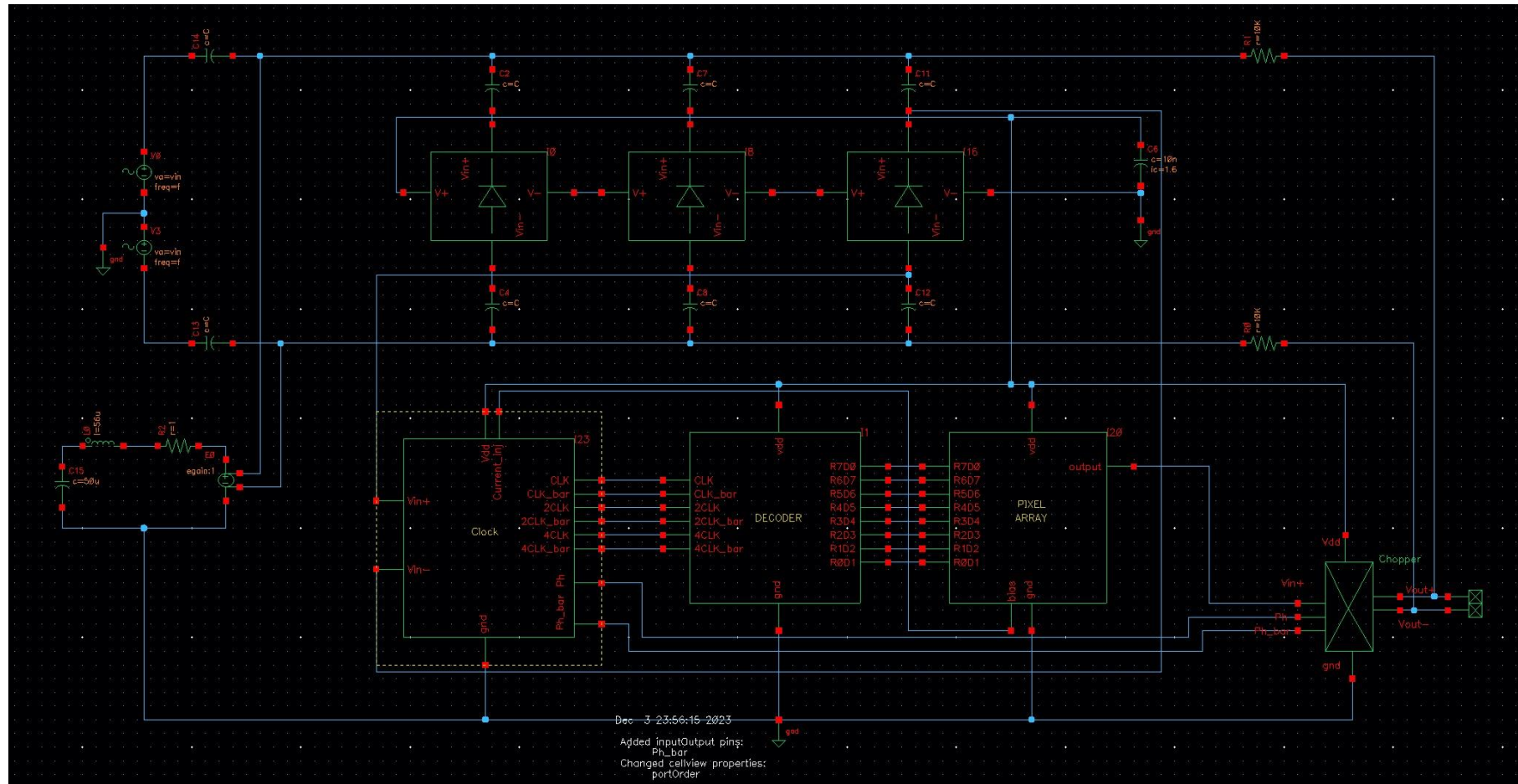


Open-loop Results

Transient Response

Name

v_dd
Data

V_diff

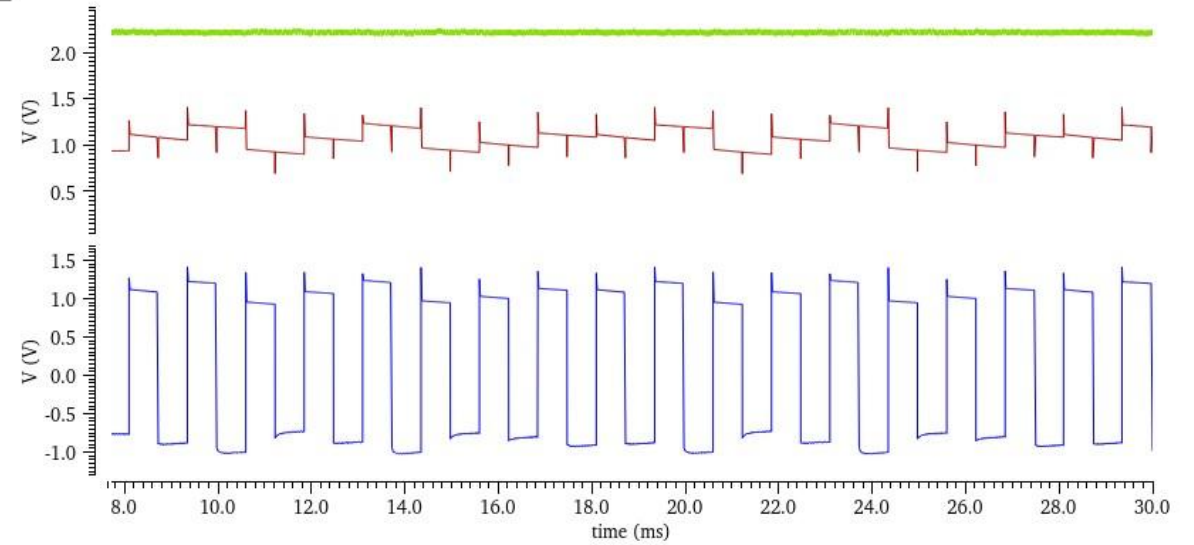

1

Signals


Name

Ph

400Hz

200Hz

100Hz

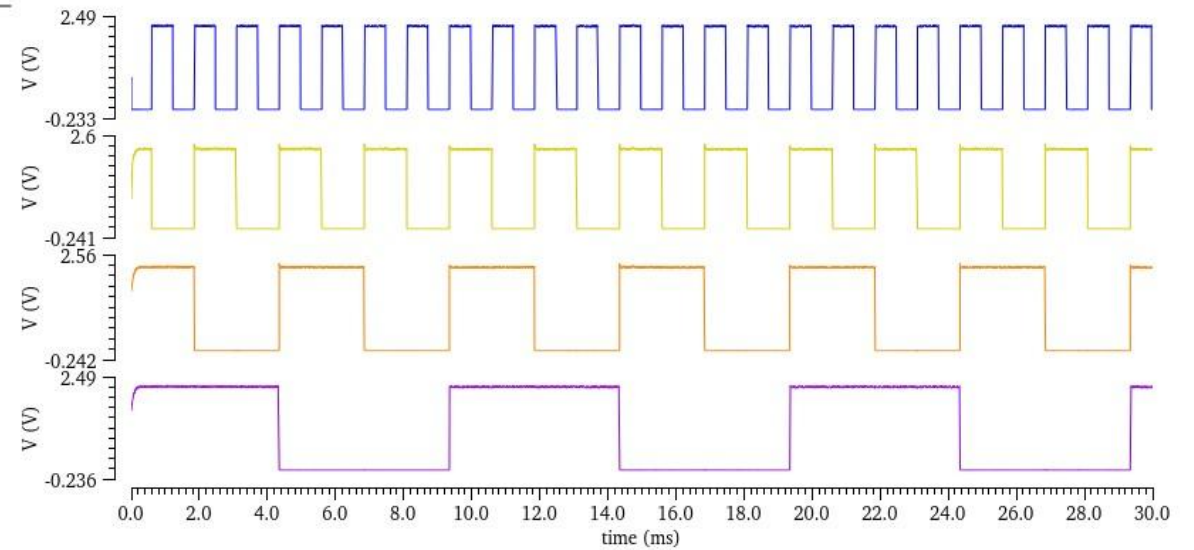

2


Closed-loop Results

Vin+:Vin-:Vout_diff:Vline_diff:Vsig_ex

Mon Dec 4 01:21:58 2023 1

Name


Vline_diff
Vout_diff

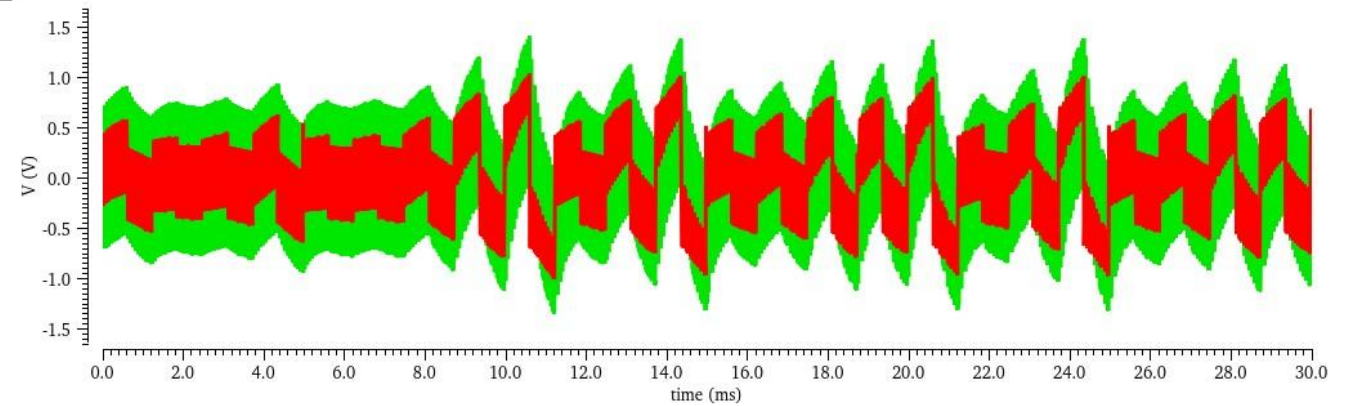

Vline_diff

Name Vis

Vline_diff
Vsig_ex

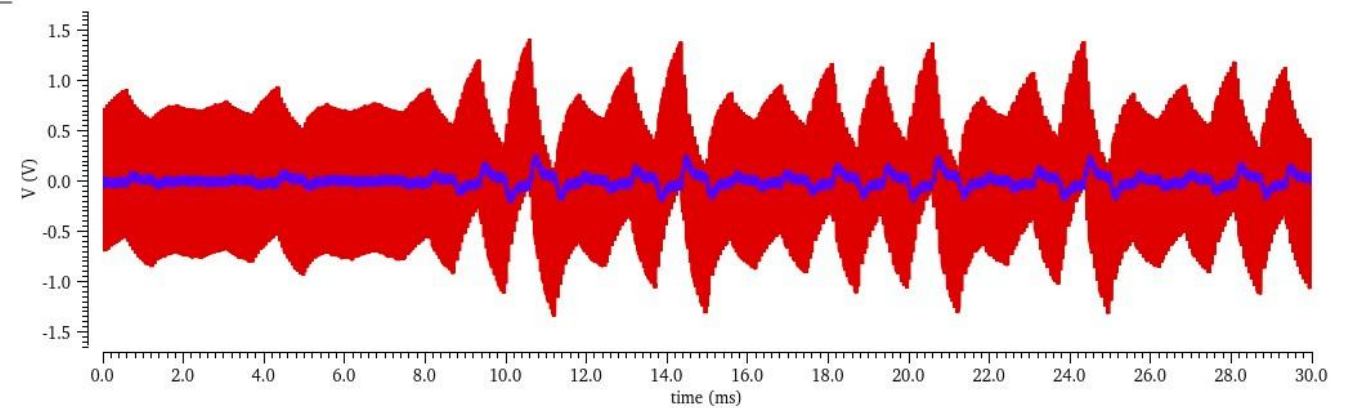

2

Reference

[1]The Trustees of Princeton University. (n.d.). *Related news*. Princeton University. <https://engineering.princeton.edu/news/2021/11/29/researchers-shrink-camera-size-salt-grain>

[2]R. K. Henderson, E. A. G. Webster, R. Walker, J. A. Richardson and L. A. Grant, "A 3×3, 5μm pitch, 3-transistor single photon avalanche diode array with integrated 11V bias generation in 90nm CMOS technology," 2010 International Electron Devices Meeting, San Francisco, CA, USA, 2010, pp. 14.2.1-14.2.4, doi: 10.1109/IEDM.2010.5703359.

[3]Y. Lu et al., "A Wide Input Range Dual-Path CMOS Rectifier for RF Energy Harvesting," in IEEE Transactions on Circuits and Systems II: Express Briefs, vol. 64, no. 2, pp. 166-170, Feb. 2017, doi: 10.1109/TCSII.2016.2554778.

[4]E. Peeters, B. Puers, W. Sansen, J. Gybels, P. de Sutter, A two-wire, digital output multichannel microprobe for recording single-unit neural activity, Sensors and Actuators B: Chemical, Volume 4, Issues 1–2, 1991, Pages 217-223, ISSN 0925-4005, [https://doi.org/10.1016/0925-4005\(91\)80201-T](https://doi.org/10.1016/0925-4005(91)80201-T).